

 


 - 11.12** A gated latch (G-L flip-flop) behaves as follows: If  $G = 0$ , the flip-flop does not change state. If  $G = 1$ , the next state of the flip-flop is equal to the value of  $L$ .
- (a) Derive the characteristic (next-state) equation for the flip-flop.
- (b) Show how an S-R flip-flop can be converted to a G-L flip-flop by adding gate(s) and inverters(s). *Hint:* What values must  $S$  and  $R$  have so that the flip-flop will be set and reset at the proper time when  $G = 1$ ? How can you prevent the flip-flop from changing state when  $G = 0$ ?
- 11.13** (a) Complete the following timing diagram for the flip-flop of Fig. 11-20.



 - (b) Complete the timing diagram for the following circuit. Note that the CK inputs on the two flip-flops are different.



**11.15** A set-dominant flip-flop is similar to the reset-dominant flip-flop of Problem 11.14 except that the input combination  $S = R = 1$  sets the flip-flop. Repeat Problem 11.14 for a set-dominant flip-flop.

**5.2** Construct a  $JK$  flip-flop, using a  $D$  flip-flop, a two-to-one-line multiplexer, and an inverter. (HDL—see Problem 5.34.)

**5.3** Show that the characteristic equation for the complement output of a  $JK$  flip-flop is

$$Q'(t+1) = J'Q' + KQ$$

**5.4** A  $PN$  flip-flop has four operations, no change, clear to 0, set 1 and complement, when inputs  $P$  and  $N$  are 00, 01, 10, and 11, respectively.

- |  |  |
|--|--|
| (a) Tabulate the characteristic table. | (b)* Derive the characteristic equation.                             |
| (c) Tabulate the excitation table.     | (d) Show how the $PN$ flip-flop can be converted to a $D$ flip-flop. |

**5.5** Explain the differences among a truth table, a state table, a characteristic table, and an excitation table. Also, explain the difference among a Boolean equation, a state equation, a characteristic equation, and a flip-flop input equation.

**5.6** A sequential circuit with two  $D$  flip-flops  $A$  and  $B$ , two inputs  $x$  and  $y$ , and one output  $z$  is specified by the following next-state and output equations (HDL—see Problem 5.35):

$$A(t+1) = x'y + xB$$


$$B(t+1) = x'A + xB$$

$$z = A$$

- Draw the logic diagram of the circuit.
- List the state table for the sequential circuit.
- Draw the corresponding state diagram.

**5.8\***

Derive the state table and the state diagram of the sequential circuit shown in Fig. P5.8. Explain the function that the circuit performs. (HDL—see Problem 5.36.)

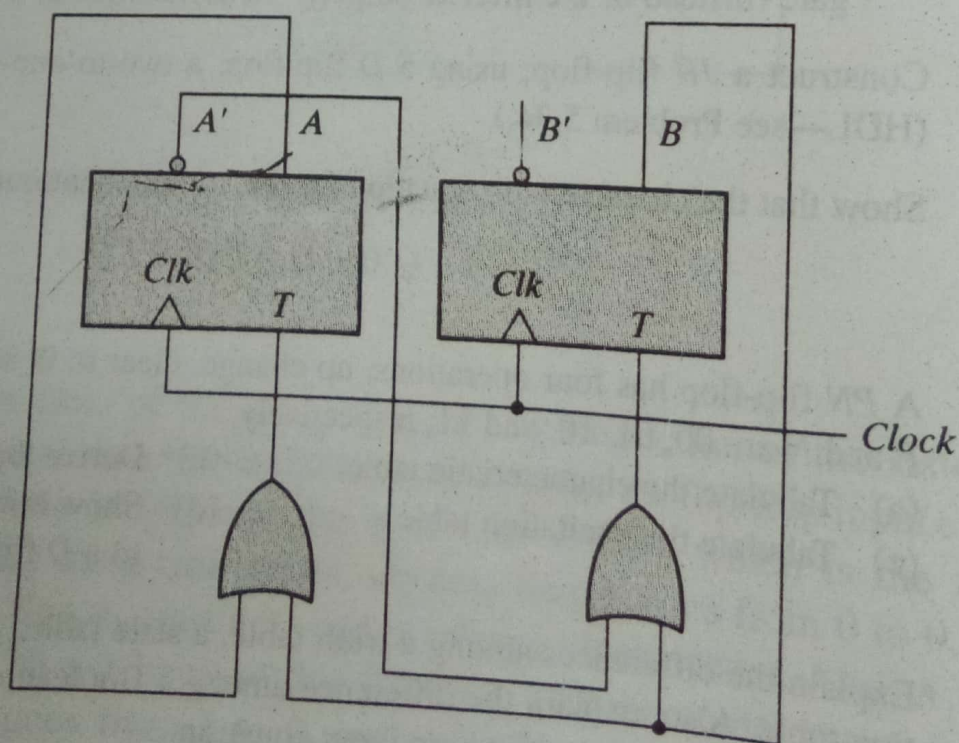

**FIGURE P5.8**



**5.10** A sequential circuit has two  $JK$  flip-flops  $A$  and  $B$ , two inputs  $x$  and  $y$ , and one output  $z$ . The flip-flop input equations and circuit output equation are

$$J_A = Bx + B'y'$$

$$K_A = B'xy'$$

$$J_B = A'x$$

$$K_B = A + xy'$$

$$z = Ax'y' + Bx'y'$$

- (a) Draw the logic diagram of the circuit.
- (b) Tabulate the state table.
- (c)\* Derive the state equations for  $A$  and  $B$ .