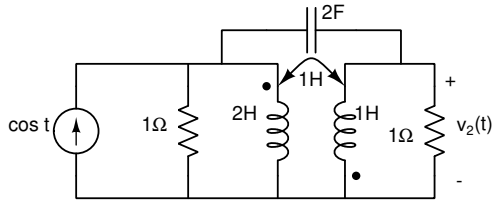



# EC2015 Electric Circuits and Networks - Tutorial 8

October 11<sup>th</sup>, 2019


1. Write nodal equations and find  $v_2(t)$ .



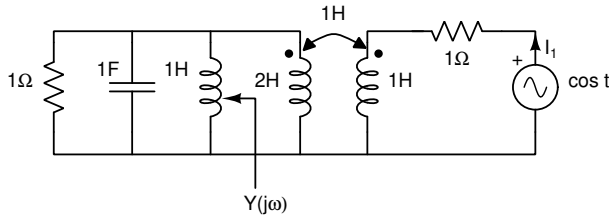2. Find  $Y(j\omega)$  and the admittance as seen by the voltage source.




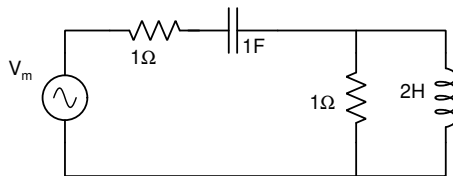3. Draw the phasor diagram showing all voltages and currents with respect to the input. Assume  $\omega = 1\text{rad/s}$ .



4. In the circuit below  $R_L = R = \sqrt{L/C}$ .

Draw a complete phasor diagram showing all voltages and currents for the condition  $|I_L| = |I_C|$ . Assume this frequency is  $\omega_1$ . If the frequency increases from  $\omega_1$  to  $\omega_2$ , how will the phasor diagram change?

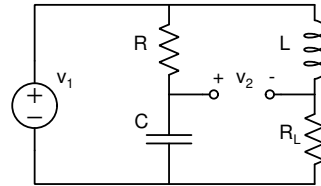

5. Use superposition and find the average power dissipated in the resistors.  $\omega = 60\text{rad/s}$ .

