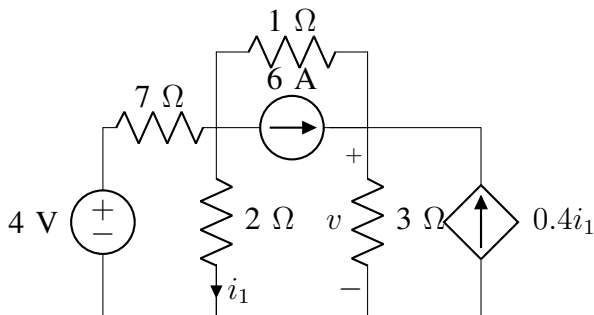


# EC2015 Electric Circuits and Networks - Tutorial 6


September 20, 2019

**Topics covered—** Superposition theorem, Source transformation theorem, Thevenin theorem, Norton theorem.

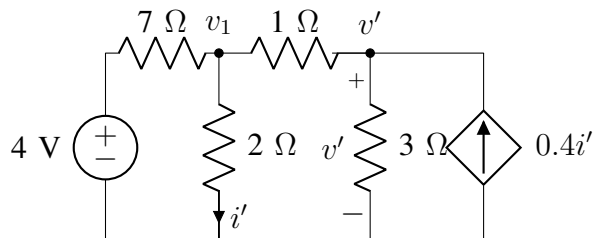1. Employ superposition to determine the individual contribution from each independent source to the voltage  $v$  and  $i_1$  as labeled in the circuit. Compute the power absorbed by the 2 Ohm resistor.



When voltage source alone acting, the circuit will modified as shown below



$$\frac{v_1 - 4}{7} + \frac{v_1}{2} + \frac{v_1 - v'}{1} = 0$$

$$\frac{v' - v_1}{1} + \frac{v'}{3} - 0.4i' = 0$$

here

$$i' = \frac{v_1}{2}$$

After substituting  $i_1$  in above equations can written as,

$$\begin{bmatrix} \frac{1}{7} + \frac{1}{2} + 1 & -1 \\ -1 - 0.2 & \frac{1}{3} + 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} -4 \\ 0 \end{bmatrix}$$


By solving

$$v_1 = 0.769 \text{ V}, v' = 0.692 \text{ V}$$

and

$$i' = \frac{v_1}{2} = 0.385 \text{ A}$$

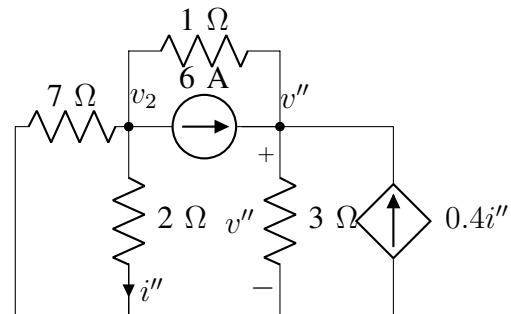When current source alone acting, the circuit will modified as shown below



$$\frac{v_2}{7} + \frac{v_2}{2} + \frac{v_2 - v''}{1} + 6 = 0$$

$$\frac{v'' - v_2}{1} + \frac{v''}{3} - 0.4i'' - 6 = 0$$

here

$$i'' = \frac{v_2}{2}$$

After substituting  $i''$  in above equations,

$$\begin{bmatrix} \frac{1}{7} + \frac{1}{2} + 1 & -1 \\ -1 - 0.2 & \frac{1}{3} + 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} -6 \\ 6 \end{bmatrix}$$

By solving these equations

$$v_2 = -2.02 \text{ V}, v'' = 2.68 \text{ V}$$

and

$$i'' = \frac{v_2}{2} = -1.01 \text{ A}$$

Therefore

$$v = v' + v'' = 0.69 + 2.68 = 3.37 \text{ V}$$


$$i = i' + i'' = 0.385 - 1.01 = -0.625 \text{ A}$$

Power dissipated in 2Ω is



$$P_{2\Omega} = i^2 * 2 = 0.782 \text{ W}$$

2. For the following circuit, the current source  $i_2$  is used to adjust the relationship between the input and output. Determine values of the current  $i_2$  and the resistance  $R$ , that cause the output to be related to the input by the equation

$$v_o = -0.5i_1 + 4$$

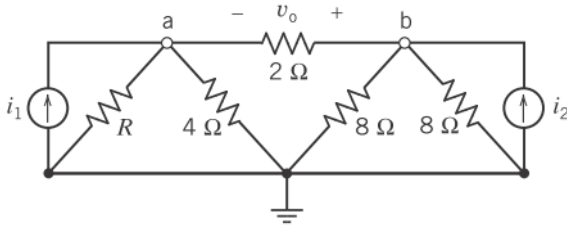

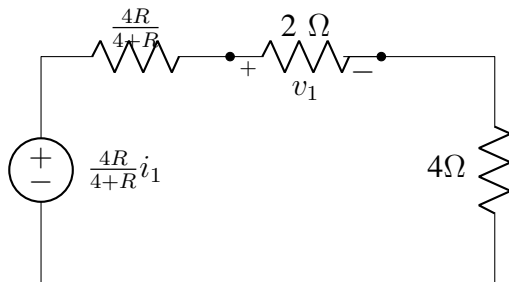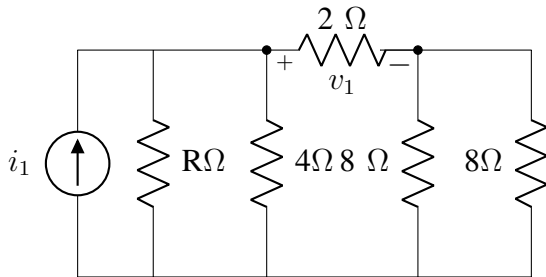When  $i_1$  alone acting, the circuit can be redrawn as below The circuit can be redrawn as



By applying voltage division rule

$$v_1 = \frac{2}{2 + 4 + \frac{4R}{4+R}} \frac{4R}{4+R} i_1 = \frac{8R}{24 + 10R}$$

When  $i_2$  alone acting, the circuit can be redrawn as below


By applying voltage division rule

$$v_2 = \frac{2}{2 + 4 + \frac{4R}{4+R}} i_2 = \frac{32 + 8R}{24 + 10R} i_2$$


Now

$$v_o = -v_1 + v_2$$

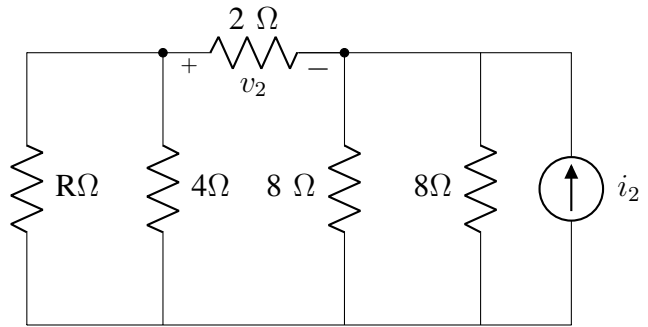
$$-0.5i_1 + 4 = -\frac{8R}{24 + 10R}i_1 + \frac{32 + 8R}{24 + 10R}i_2$$



The circuit can be redrawn as

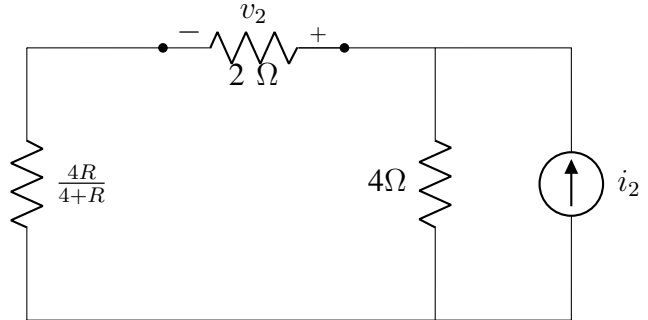

The circuit can be redrawn as

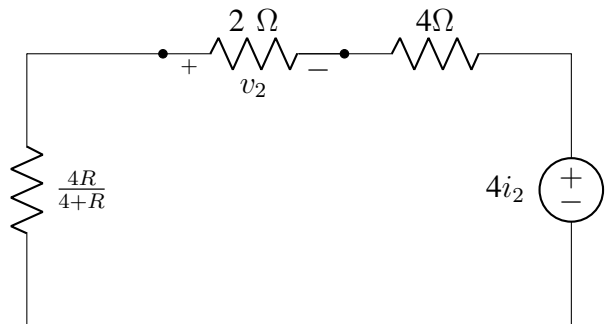


By equating

$$\frac{8R}{24 + 10R} = 0.5, \quad \frac{32 + 8R}{24 + 10R} i_2 = 4$$


By solving,

$$R = 4\Omega \text{ and } i_2 = 4A$$

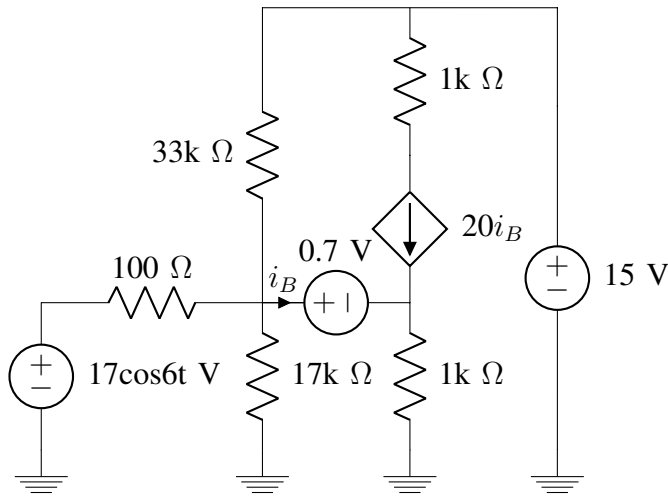3. The following circuit is a commonly used as a model for bipolar junction transistor amplifier. Find the value of base current  $i_B$  using superposition theorem.



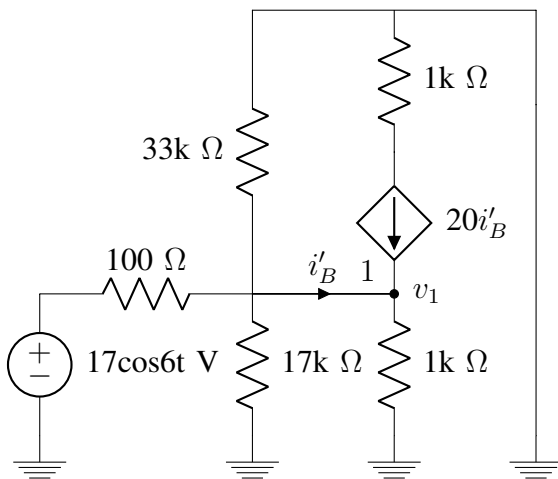When the  $17\cos 6t$  source alone acting, the circuit is redrawn as



By writing KCL at node 1:

$$i'_B + 20i'_B = \frac{v_1}{1k}$$

and

$$v_1 \left( \frac{1}{100} + \frac{1}{33k} + \frac{1}{17k} + \frac{1}{1k} \right) - 20i'_B - \frac{17\cos 6t}{100} = 0$$


by substituting  $i'_B$  in this equation

$$v_1 \left( \frac{1}{100} + \frac{1}{33k} + \frac{1}{17k} + \frac{1}{1k} - \frac{20}{21k} \right) = \frac{17\cos 6t}{100}$$

$$v_1 = 16.77\cos 6t$$

$$i'_B = \frac{v_1}{21k} = 0.7986 \cos 6t \text{ mA}$$

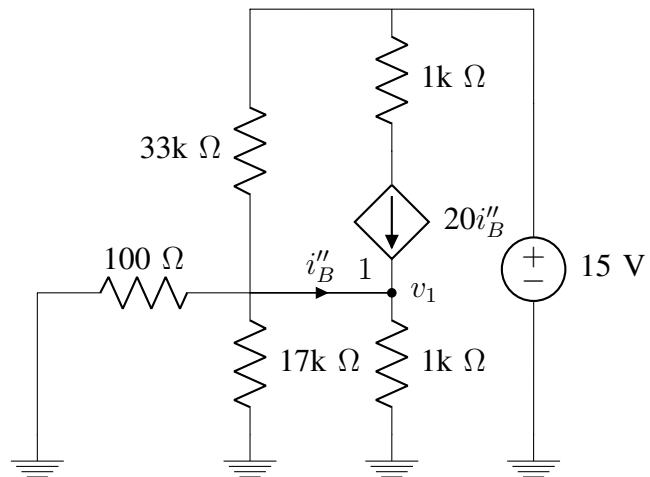When the 15 V source alone acting, the circuit is redrawn as



By writing KCL at node 1:

$$i''_B + 20i''_B = \frac{v_1}{1k}$$

and

$$v_1 \left( \frac{1}{100} + \frac{1}{33k} + \frac{1}{17k} + \frac{1}{1k} \right) - 20i''_B - \frac{15}{33k} = 0$$


by substituting  $i''_B$  in this equation

$$v_1 \left( \frac{1}{100} + \frac{1}{33k} + \frac{1}{17k} + \frac{1}{1k} - \frac{20}{21k} \right) = \frac{15}{33k}$$

$$v_1 = 44.84 \text{ mV}$$

$$i''_B = \frac{v_1}{21k} = 2.13 \text{ } \mu\text{A}$$

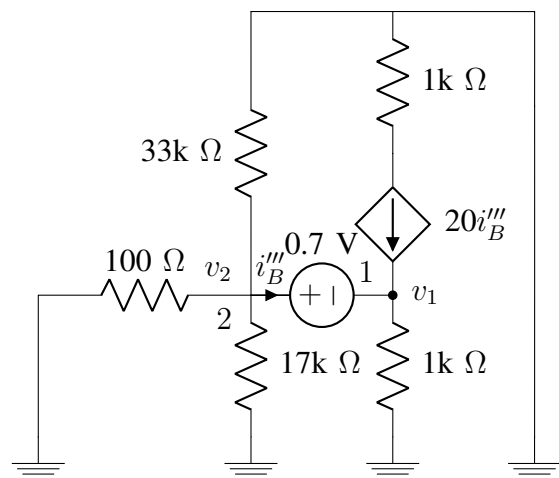When the 0.7 V source alone acting, the circuit is redrawn as



By writing KCL at node 1:

$$i_B''' + 20i_B''' = \frac{v_1}{1k}$$

and

$$v_2 - v_1 = 0.7$$

The super node equation is:

$$v_2\left(\frac{1}{100} + \frac{1}{33k} + \frac{1}{17k}\right) + v_1\left(\frac{1}{1k}\right) - 20i_B''' = 0$$

by substituting  $i_B'''$  in this equation

$$v_2\left(\frac{1}{100} + \frac{1}{33k} + \frac{1}{17k}\right) + v_1\left(\frac{1}{1k} - \frac{20}{21k}\right) = 0$$

By solving

$$v_1 = -0.6967 \text{ V and } v_2 = 0.003 \text{ V}$$


$$i_B''' = \frac{v_1}{21k} = -33.17 \mu A$$

Now

$$i_B = i_B' + i_B'' + i_B''' = 798.6 \cos 6t - 33.17 + 2.13 \mu A$$

$$i_B = 798.6 \cos 6t - 31.04 \mu A$$

Alternative method:

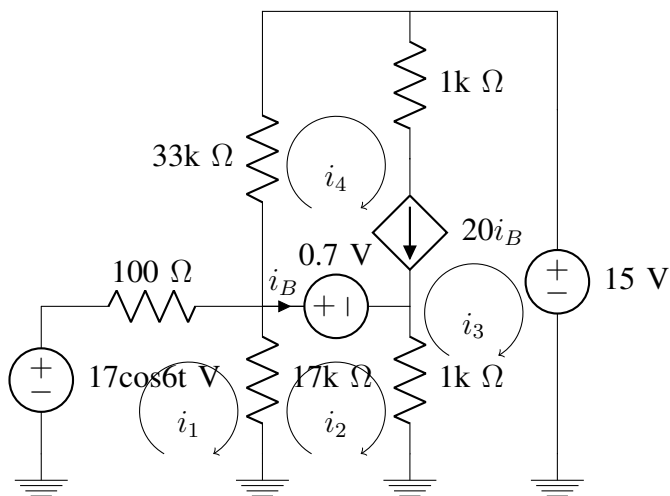

Here

$$i_2 - i_4 = i_B$$

$$i_4 - i_3 = 20i_B$$

By applying Kvl to loop 1:

$$-17\cos 6t + 100i_1 + 17k(i_1 - i_2) = 0$$

By applying Kvl to loop 1:

$$17k(i_2 - i_1) + 0.7 + 1k(i_2 - i_3) = 0$$

By writing super mesh equation:

$$17k(i_2 - i_1) + 33ki_4 + 15 = 0$$

We can write these equation in matrix form as




$$\begin{bmatrix} 17.1k & -17k & 0 & 0 & 0 \\ -17k & 18k & -1k & 0 & 0 \\ -17k & 17k & 0 & 33k & 0 \\ 0 & 1 & 0 & -1 & -1 \\ 0 & 0 & -1 & 1 & -20 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_B \end{bmatrix} = \begin{bmatrix} 17\cos 6t \\ -0.7 \\ -15 \\ 0 \\ 0 \end{bmatrix}$$


By solving above matrices using Gauss elimination method,

$$i_B = 798.6 \cos 6t - 31.04 \mu A$$

4. For the given circuits here, compute the voltage  $v_o$  (in the 1st circuit) and  $i_x$  (in the 2nd circuit) using source transformation technique.

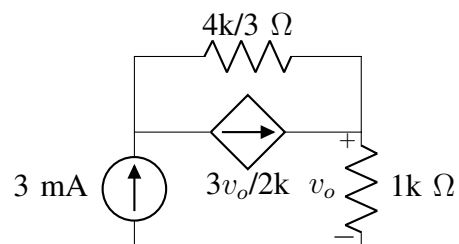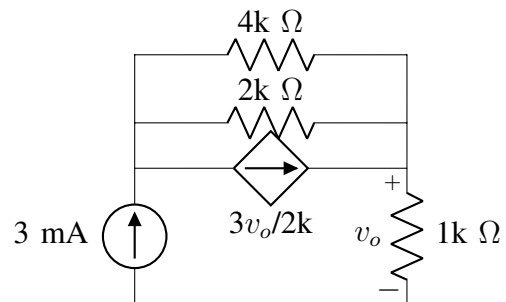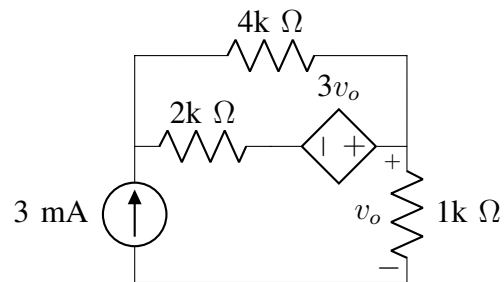a. By applying source transformation technique on dependent source, the circuit modifies as shown below




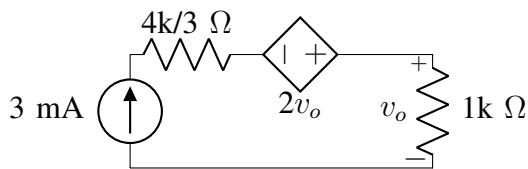


As all elements are in series, the current flowing through  $1k\ \Omega$  resistor is 3 mA. Therefore,

$$v_o = 3m * 1k = 3\text{ V}$$


b.

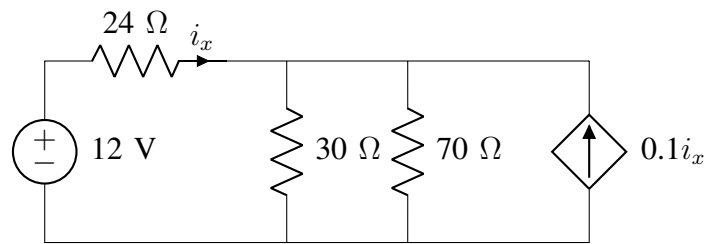

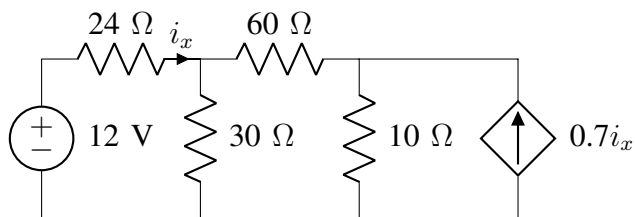
The  $70\Omega$  and  $30\Omega$  are in parallel, so these two can replace with  $21\Omega$  as shown below



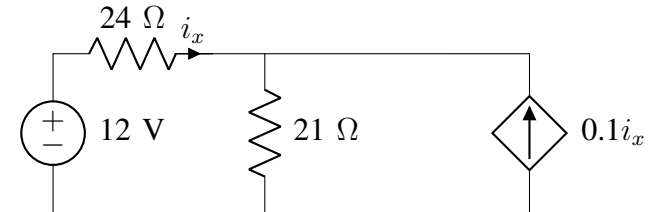
By applying source transformation technique on dependent source, the circuit modifies as shown below. As we need to find the value of  $i_x$ . So, the branch which is having  $i_x$  is not disturbed throughout the process.



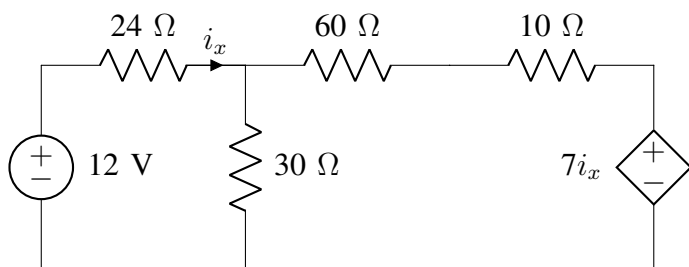By applying source transformation technique on dependent source, the circuit modifies as shown below



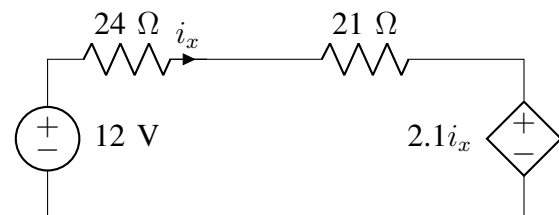The  $60\Omega$  and  $10\Omega$  are in series, so these two can replace with  $70\Omega$  as shown below




By writing KVL to the loop:

$$-12 + 24i_x + 21i_x + 2.1i_x = 0$$

$$47.1i_x = 12$$

$$i_x = 0.254A$$

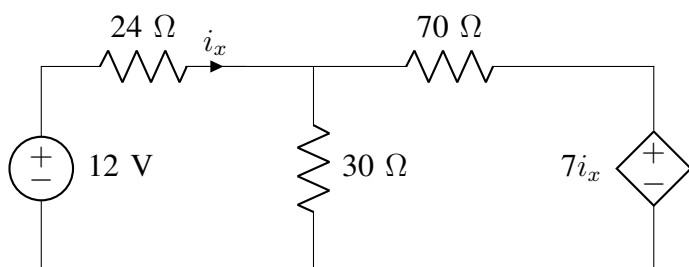

By applying source transformation technique on dependent source, the circuit modifies,