

# Model Answers -

Name:

Roll Number:

## EE2001 Quiz I

Monday, 19/02/18

Closed book, 50 mins, 20 points

Remember...

- Make reasonable assumptions when in doubt. However, you should show all steps in additional sheets and justify assumptions for full credit. **Provide final answers ONLY in the space provided.**

1. In a particular number system of base  $r$ , the roots of the equation  $5x^2 + 50x + 125 = 0$  are given by  $x = -8$  and  $x = -5$ . The value of  $r$  is **13**. (2 pts)

$$(x+8)(x+5) = 0 \Rightarrow x^2 + 13x + 40 = 0 \Rightarrow 5x^2 + 65x + 200 = 0.$$

$$5r = 65 \Rightarrow r = 13; \text{ Also, } 1 \times 13^2 + 2 \times 13 + 5 = 200. \text{ (Confirmed).}$$


2. Simplify the following Boolean function and implement the same using NAND-AND gates:

$$F(w, x, y, z) = \Pi(4, 6, 8, 9, 10, 12, 13, 14)$$

(3 pts)

$w \backslash x$	00	01	11	10
00				
01	0			0
11	0	0		0
10	0	0		0

$$F' = wy' + xz' + wz'$$

 


3. Implement the following Boolean functions using ONLY three half-adder circuits: (4 pts)

(i)  $D = A \oplus B \oplus C$

(ii)  $E = A'BC + AB'C$

(iii)  $F = ABC' + (A' + B')C$

(iv)  $G = ABC$

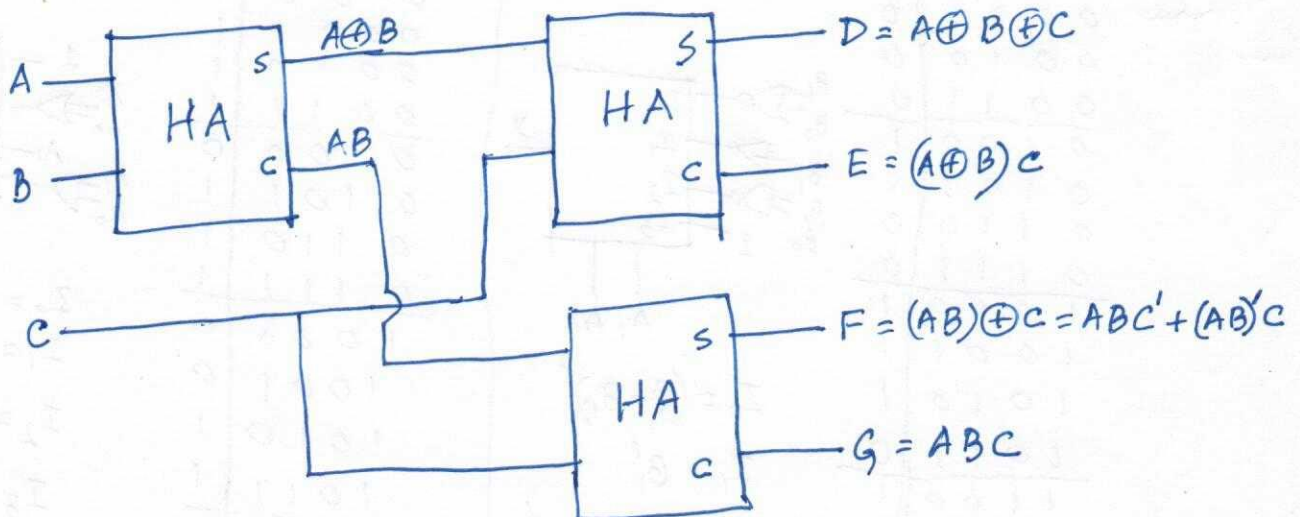



4. (a) Obtain Boolean expressions for the carry bits ( $C_1, C_2, C_3, C_4$ ) of a 4-bit carry look ahead adder.

$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

$$C_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$$

$$G_i = A_i B_i$$

$$P_i = A_i \oplus B_i$$

- (b) Assuming that the exclusive-OR gate has a propagation delay of 20 ns and all other gates have propagation delay of 10 ns, the total propagation delay for this 4-bit adder is 60 ns.

1 Ex-OR for generating  $P_i$ 's and  $G_i$ 's + 2 Gates for generating carries + 1 Ex-OR for Sum output

- (c) If two such 4-bit adders are connected to realize an 8-bit adder, the total propagation delay is 80 ns.

For the CLA for higher order bits,  $C_4$  is available after 40 ns. (1+2+2 pts)


Delay = 40 ns + 20 ns (to generate all  $C_i$ 's) + 20 ns for Sum outputs.

5. Design and draw the circuit of an 8-bit magnitude comparator realized using two 4-bit magnitude comparators and a few gates. The magnitude comparators have 3 outputs, viz.  $A = B$ ,  $A > B$  and  $A < B$ .

$$(A = B) = (A = B)_{0-3} \cdot (A = B)_{4-7}$$


$$(A > B) = (A > B)_{4-7} + (A = B)_{4-7} \cdot (A > B)_{0-3}$$
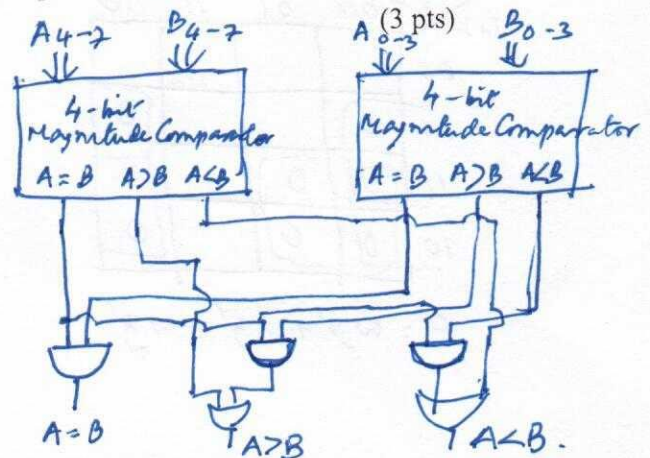
$$(A < B) = (A < B)_{4-7} + (A = B)_{4-7} \cdot (A < B)_{0-3}$$



6. Two 2-bit binary numbers  $A = A_1 A_0$  and  $B = B_1 B_0$  are fed into a 4-bit logic circuit, whose output is 1 only if  $A \geq B$ . Design and draw the circuit using one 4 x 1 MUX and some gates. (3 pts)

$A_1 A_0$	$B_1 B_0$	$Y$
00	00	1
00	01	0
00	10	0
00	11	0
01	00	1
01	01	1
01	10	0
01	11	0
10	00	1
10	01	1
10	10	1
10	11	0
11	00	1
11	01	1
11	10	1
11	11	1

 


$$I_0 = (B_1 + B_0)'$$

$$I_1 = B_1'$$

$$I_2 = (B_1 \cdot B_0)'$$

$$I_3 = 1$$

$B_1 B_0$	$A_1 A_0$	$Y$
00	00	1
00	01	1
00	10	1
00	11	1
01	00	0
01	01	1
01	10	1
01	11	1
10	00	0
10	01	0
10	10	1
10	11	0
11	00	0
11	01	0
11	10	0
11	11	0

 

$$I_0 = 1$$

$$I_1 = A_1 + A_0$$

$$I_2 = A_1$$

$$I_3 = A_1 \cdot A_0$$