

Name: _____

Roll Number: _____



EE2001 Quiz II**Monday, 02/04/18****Closed book, 50 mins, 20 points**

Remember...


- Make reasonable assumptions when in doubt. However, you should show all steps and justify assumptions for full credit. **Provide final answers ONLY in the space provided.**

1. Draw the state diagram for a Flip-Flop which has two inputs X and Y and two outputs Q and Q'. When Y = 0, the output Q_n is equal to the previous state Q_{n-1} and when Y = 1, Q_n = X. Realize the Flip-Flop using a D Flip-Flop and some gates. (4 pts)


X	Y	Q _{n-1}	Q _n
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

  

$$Q_n = XY + Q_{n-1}Y'$$

 

 2. Design and draw the circuit of a synchronous single input single output system such that the output Z = 1 with every occurrence of an input 1 following a string of at least two consecutive 0 inputs. At all other times, the output Z = 0. (4 pts)



D _A	$\overline{B}x$	$\overline{B}x$	Bx	Bx
\overline{A}				1
A	1		x	x

$$D_A = \overline{x}(A+B)$$

D _B	$\overline{A}\overline{B}x$	$\overline{A}\overline{B}x$	$\overline{A}\overline{B}x$	$\overline{A}\overline{B}x$
\overline{A}				
B	1	1	1	1


$$D_B = A\overline{B}x$$

A	B	x	\overline{A}	B^+	o/p	D _A	D _B
0	0	0	0	1	0	0	1
0	0	1	0	0	0	0	0
0	1	0	1	0	0	1	0
0	1	1	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	1	0	0

Name: _____

Roll Number: _____

 3. Design and draw the circuit of a synchronous mod-6 counter which counts from 000 in the binary sequence. Also, if any unused state occurs, the output goes to 000 at the next clock pulse. (4 pts)



binary sequence. Also in any analysis pulse.

Present state

Q_2 Q_1 Q_0

0 0 0

0 0 1

0 1 0

0 1 1

1 0 0

1 0 1

1 1 0

1 1 1

Next state

Q_2 Q_1 Q_0

0 0 1

0 1 0

0 1 1

1 0 0

1 0 1

0 0 0

0 0 0

D Flip-Flop input

D_A D_B D_C

0 0 1

0 0 1

0 1 1

1 0 0

1 0 1

0 0 0

0 0 0

T Flip-Flop

T_A T_B T_C

0 0 1

0 1 1

0 0 1

1 1 1

0 0 1

1 0 1

1 1 1

J Flip-Flop

J_A J_B J_C

0 0 1

0 1 1

0 0 1

1 1 1

0 0 1

0 1 1

0 1 1

K Flip-Flop

K_A K_B K_C

0 0 1

0 1 1

0 0 1

1 1 1

0 0 1

1 0 1

1 1 1

$T_A = AB + BC$

$Q_2Q_1 + Q_1Q_0$

$+ Q_2Q_0$

$T_B = Q_2'Q_0$

$+ Q_2Q_1$

$T_C = Q_2' + Q_1' + Q_0$

$J_A = Q_1Q_0$

$K_A = Q_1'Q_0'$

$J_B = Q_2'Q_0$

$K_B = Q_2'Q_0'$

$J_C = Q_2Q_1$

$K_C = 1$

$$D_A = Q_2'Q_1Q_0 + Q_2Q_1'Q_0'$$

$$D_B = Q_2'Q_1'Q_0 + Q_2'Q_1Q_0'$$

$$D_C = Q_2'Q_0' + Q_2Q_0'$$

$$J_A = Q_1Q_0$$

$$J_B = Q_2'Q_0$$

$$J_C = Q_2Q_1$$


$$K_A = Q_1'Q_0'$$

$$K_B = Q_2'Q_0'$$

$$K_C = 1$$

parallel data once in every 4 clock pulses and

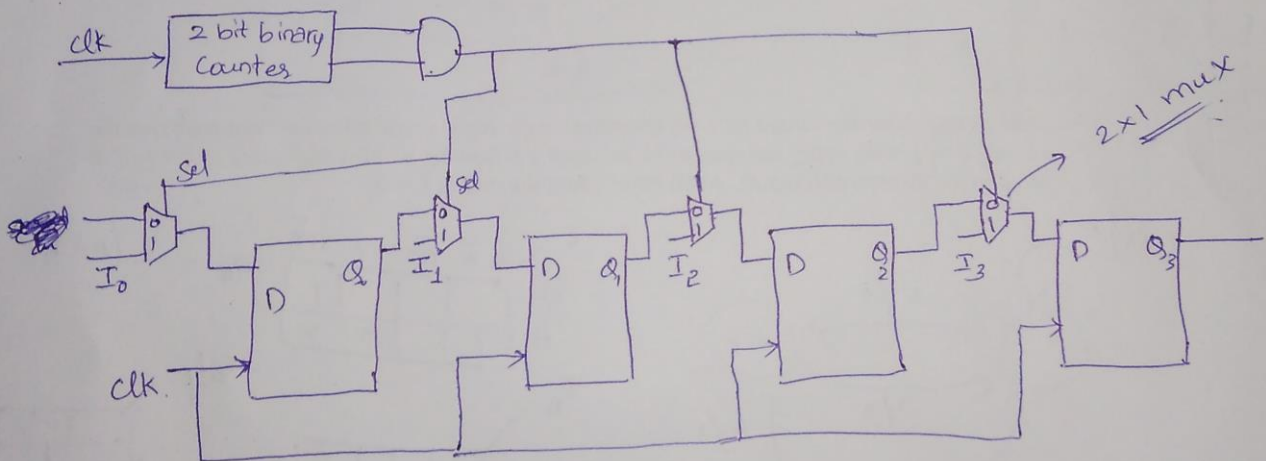4. Draw the circuit of a system which loads 4-bit parallel data once in every 4 clock pulses and outputs them as 4-bit serial data. The design must include generation of appropriate control signals to load data at proper intervals. (4 pts)



5. (a) Consider a 16 M x 8 memory constructed using the above element. The number of address lines and the input/output data lines required are 24 and 8 respectively. (2pts)
- (b) The number of AND gates required for the decoder in the above memory is 2^{24} for 1-D addressing and 2^{13} for 2-D addressing (2pts)

