
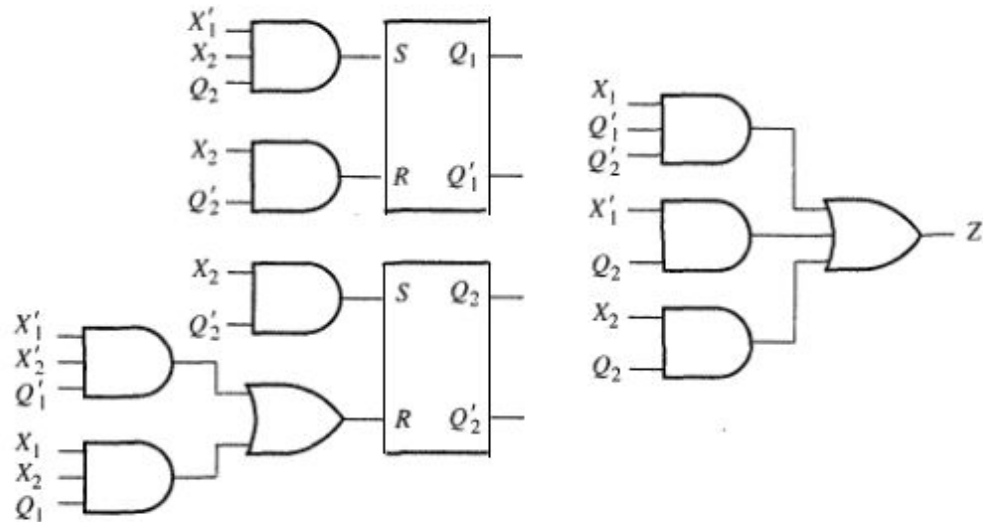


Tutorial 8

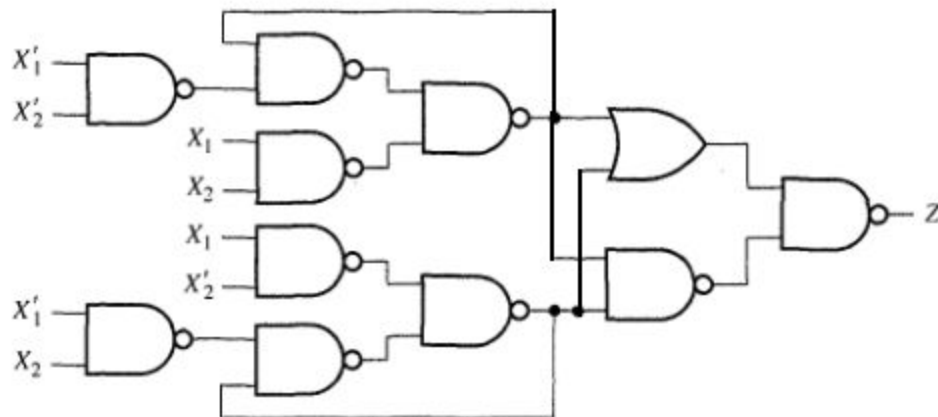
- 1) For the following network, construct a flow table and determine the output sequence. The initial state is 00 and the input sequence is $X_1X_2 = 00, 01, 11, 10, 00$.



- 2) Analyze the following network using a flow table. What is the output sequence for the following input sequence: $X_1X_2 = 00, 10, 11, 01, 11, 10, 00, 01, 00$? Indicate transients, if any, in parentheses.




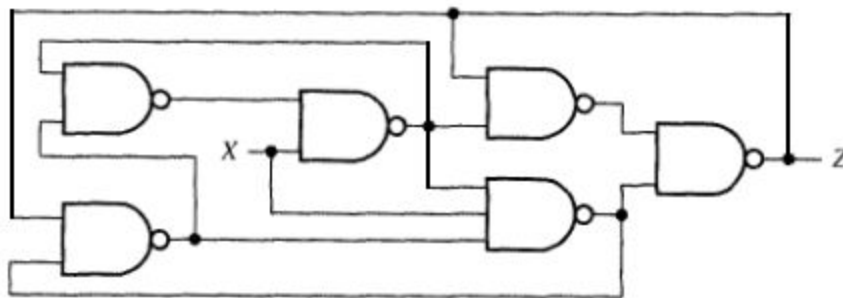- 3) (a) Analyze the following asynchronous network using a flow table. Starting in the stable total state for which $X = Z = 0$, determine the state and output sequences when the input sequence is $X = 0, 1, 0, 1, 0, 1 \dots$
- (b) Are there any races in the flow table? If so, are they critical races?



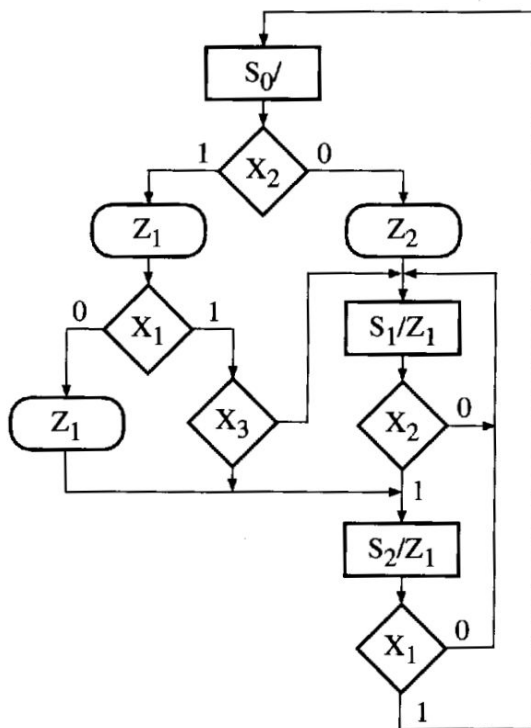4) For the following SM chart

- Use the state assignment $S_0: AB = 00$; $S_1: AB = 01$; $S_2: AB = 10$. Derive the next state and output equations by tracing link paths. Simplify these equations using the don't care state ($AB = 11$).
- Realize the chart using a PLA and D flip-flops. Give the PLA table.
- If a ROM is used instead of a PLA, what size ROM is required? Give the first five rows of the ROM table.



5)

The following SM chart is to be realized using a PLA, a 4-to-1 MUX, and a 3-bit binary counter (similar to a 74163).

- Draw a block diagram of the system.
- Make a suitable state assignment. Indicate any necessary changes on the SM chart.
- Give the PLA table.

