

Tutorial 4 Solutions

5.10 A sequential circuit has two *JK* flip-flops *A* and *B*, two inputs *x* and *y*, and one output *z*. The flip-flop input equations and circuit output equation are

$$\begin{aligned} J_A &= Bx + B'y' & K_A &= B'xy' \\ J_B &= A'x & K_B &= A + xy' \\ z &= Ax'y' + Bx'y' \end{aligned}$$

- (a) Draw the logic diagram of the circuit.
 (b) Tabulate the state table.
 (c)* Derive the state equations for *A* and *B*.

sol:

5.10 (a) $J_A = Bx + B'y'$ $J_B = A'x$
 $K_A = B'xy'$ $K_B = A + xy'$ $z = Ax'y' + Bx'y'$

(b)

Present state		Inputs		Next state		Output	FF Outputs			
<i>A</i>	<i>B</i>	<i>x</i>	<i>y</i>	<i>A</i>	<i>B</i>	<i>z</i>	J_A	K_A	J_B	K_B
0	0	0	0	1	0	0	1	0	0	0
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	1	0	1	1	1	1
0	0	1	1	0	1	0	0	0	1	0
0	1	0	0	0	1	1	0	0	0	0
0	1	0	1	0	1	0	0	0	0	0
0	1	1	0	1	0	0	1	0	1	0
0	1	1	1	1	1	0	1	0	1	0
1	0	0	0	1	0	0	1	0	0	1
1	0	0	1	1	0	0	0	0	0	1
1	0	1	0	0	0	0	1	1	0	1
1	0	1	1	1	0	0	0	0	0	1
1	1	0	0	1	0	1	0	0	0	1
1	1	0	1	1	0	0	0	0	0	1
1	1	1	0	1	0	0	1	0	0	1
1	1	1	1	1	0	1	1	0	0	1

(c)

<i>AB</i>		<i>xy</i>				<i>B</i>
		00	01	11	10	
<i>A</i>	00	m_0 1	m_1	m_3	m_2 1	
	01	m_4	m_5	m_7 1	m_6 1	
	11	m_{12} 1	m_{13} 1	m_{15} 1	m_{14} 1	
	10	m_8 1	m_9 1	m_{11} 1	m_{10}	


$$A(t+1) = Ax' + Bx + Ay + A'B'y'$$

<i>AB</i>		<i>xy</i>				<i>B</i>
		00	01	11	10	
<i>A</i>	00	m_0	m_1	m_3 1	m_2 1	
	01	m_4 1	m_5 1	m_7 1	m_6	
	11	m_{12}	m_{13}	m_{15}	m_{14}	
	10	m_8	m_9	m_{11}	m_{10}	

$$B(t+1) = A'B'x + A'B'(x' + y)$$

5.2) Construct a JK flip flop using a D flip flop, 2 x 1 mux and an inverter
sol:

5.2

 

5.8* Derive the state table and the state diagram of the sequential circuit shown in Fig. P5.8. Explain the function that the circuit performs. (HDL—see Problem 5.36.)

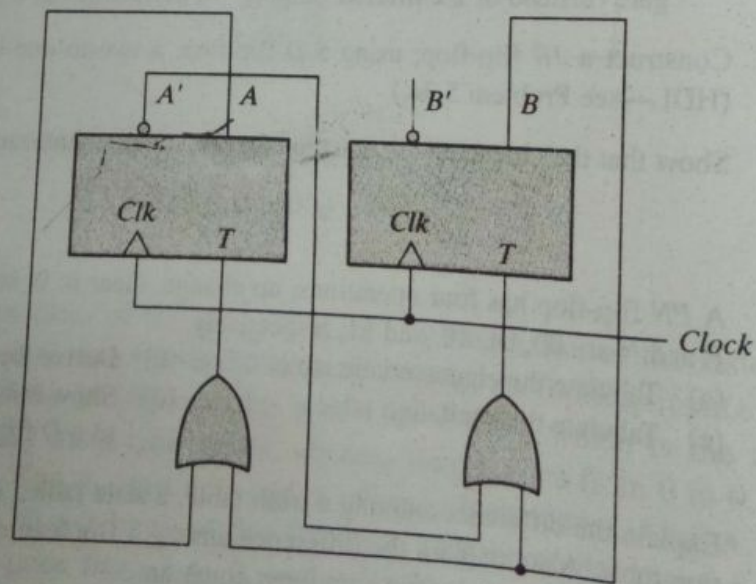


FIGURE P5.8

sol:



5.8 A counter with a repeated sequence of 00, 01, 10.

Present state		Next state		FF Inputs	
A	B	A	B	T_A	T_B
0	0	0	0	0	1
0	1	1	0	1	1
1	0	0	0	1	0
1	1	0	0	1	1

$$T_A = A + B$$

$$T_B = A' + B$$

Repeated sequence:

  

5.4

A *PN* flip-flop has four operations, no change, clear to 0, set 1 and complement, when inputs *P* and *N* are 00, 01, 10, and 11, respectively.

(a) Tabulate the characteristic table.

(b)* Derive the characteristic equation.

(c) Tabulate the excitation table.

(d) Show how the *PN* flip-flop can be converted to a *D* flip-flop.

sol:


5.4

(a)

P	N	Q(t+1)
0	0	0
0	1	Q(t)
1	0	Q'(t)
1	1	1

(b)

P	N	Q(t)	Q(t+1)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

 

(c)

Q(t)	Q(t+1)	P	N
0	0	0	x
0	1	1	x
1	0	x	0
1	1	x	1

(d) Connect P and N together.

- 5.6** A sequential circuit with two D flip-flops A and B , two inputs x and y , and one output z is specified by the following next-state and output equations (HDL—see Problem 5.35):

$$A(t+1) = x'y + xB$$


$$B(t+1) = x'A + xB$$

$$z = A$$

- Draw the logic diagram of the circuit.
- List the state table for the sequential circuit.
- Draw the corresponding state diagram.

sol:


5.6 (a)

 


(b)

Present state		Inputs		Next state		Output
A	B	x	y	A	B	z
0	0	0	0	0	0	0
0	0	0	1	1	0	0
0	0	1	0	0	0	0
0	0	1	1	0	0	0
0	1	0	0	0	1	1
0	1	0	1	1	1	1
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	0	0	0
1	0	0	1	1	0	0
1	0	1	0	1	1	0
1	0	1	1	1	1	0
1	1	0	0	0	1	1
1	1	0	1	1	1	1
1	1	1	0	1	1	1
1	1	1	1	1	1	1


(c)

 

11.13 b)

 

sol:

 

11.15 A set-dominant flip-flop is similar to the reset-dominant flip-flop of Problem 11.14 except that the input combination $S = R = 1$ sets the flip-flop. Repeat Problem 11.14 for a set-dominant flip-flop.

sol:

11.15 (a)

S	R	Q	Q ⁺
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

		S	
		0	1
R \ Q	00	0	1
	01	1	1
	11	0	1
	10	0	1

$Q^+ = S + R'Q$

11.15 (b) A set-dominant FF from an S-R FF—The arrangement will ensure that when $S = R = 1$, $S_I = 1$, $R_I = 0$, and $Q^+ = 1$.

