

Tutorial 5 Solutions

1.Design a 3-bit counter which counts in the sequence:

001, 011, 010, 110, 111, 101, 100, 001,...

a) Use clocked D flip-flops.

b) Use clocked T flip-flops.

sol:

(a)

CBA	$C^+B^+A^+$
000	X X X
001	0 1 1
010	1 1 0
011	0 1 0
100	0 0 1
101	1 0 0
110	1 1 1
111	1 0 1

$C^+ = CA + BA'$

$B^+ = C' + BA'$

$A^+ = C'B' + CB + B'A'$
 $A^+ = C'B' + CB + CA'$

For D flip-flop: 000 goes to 011 because $D_C D_B D_A = 011$

(b)

$T_C = C'A' + B'A'$

$T_B = C'B' + CBA$

$T_A = C'BA + CB' + CA'$

For T flip-flop: 000 goes to 110 because $T_A T_B T_C = 110$


2.Repeat above Problem for the sequence using clocked JK flip-flops.

001, 100, 101, 111, 110, 010, 011, 001,...

Sol:

$JA = B'$, $KA = BC'$; $JB = AC$, $KB = A'C$; $JC = A' + B'$, $KC = A'B' + AB$

 4. (a) For the following sequential network, find the next-state equation or map for each flip-flop. Using these next-state equations or maps, construct a (Moore) state table and graph for the network.
- (b) What is the output sequence when the input sequence is $X = 01100$?
- (c) Draw a timing diagram for the input sequence in (b). Show P_c , X , A , B , and Z . Assume that the input changes between clock pulses.



sol:


(a) $A^+ = A(B' + X) + A'(BX' + B'X)$ $B^+ = AB'X + B(A' + X')$

Present State AB	Next State ($A^+ B^+$)		Z
	$x = 0$	$x = 1$	
00	00	10	0
01	11	01	0
11	01	10	1
10	10	11	0

This is a Moore machine.


(b) $Z = (0)00101$

(c)

 

5. Design a four-bit shift register with parallel load using D flip-flops. There are two control inputs: shift and load. When shift = 1, the content of the register is shifted by one position. New data are transferred into the register when load = 1 and shift = 0. If both control inputs are equal to 0, the content of the register does not change.

sol:

 

6. A flip-flop has a 3 ns delay from the time the clock edge occurs to the time the output is complemented. What is the maximum delay in a 10-bit binary ripple counter that uses these flip-flops? What is the maximum frequency at which the counter can operate reliably?

sol: The worst case is when all 10 flip-flops are complemented.

The maximum delay is $10 \times 3\text{ ns} = 30\text{ ns}$.

The maximum frequency is $10^9 / 30 = 33.3\text{ MHz}$

7. Design a serial 2's complementer with a shift register and a flip-flop. The binary number is shifted out from one side and its 2's complement shifted into the other side of the shift register?

sol:

Note that $y = x$ if $Q = 0$, and $y = x'$ if $Q = 1$. Q is set on the first 1 from x .

Note that $x \oplus 0 = x$, and $x \oplus 1 = x'$.

