

**EE2001-Tutorial 2**  
**Date: 30<sup>th</sup> January 2018**  
**Gate-Level Minimization and Some Combinational Logic**

1) Simplify the following Boolean functions, using Karnaugh maps:

- (a)  $F(x, y, z) = \Sigma(2, 3, 6, 7)$
- (b)  $F(A, B, C, D) = \Sigma(4, 6, 7, 15)$
- (c)  $F(A, B, C, D) = \Sigma(3, 7, 11, 13, 14, 15)$
- (d)  $F(w, x, y, z) = \Sigma(2, 3, 12, 13, 14, 15)$
- (e)  $F(w, x, y, z) = \Sigma(11, 12, 13, 14, 15)$
- (f)  $F(w, x, y, z) = \Sigma(8, 10, 12, 13, 14)$

2) Simplify the following Boolean expressions, using four variable K-maps:

- (a)  $w'z + xz + x'y + wx'z$
- (b)  $AD' + B'C'D + BCD' + BC'D$
- (c)  $AB'C + B'C'D' + BCD + ACD' + A'B'C + A'BC'D$
- (d)  $wxy + xz + wx'z + w'x$

3) Find the minterms of the following Boolean expressions:

- (a)  $xy + yz + xy'z$
- (b)  $C'D + ABC' + ABD' + A'B'D$
- (c)  $wyz + w'x' + wxz'$
- (d)  $A'B + A'CD + B'CD + BC'D'$

4) Find all the prime implicants for the following Boolean functions, and determine which are essential:

- (a)  $F(w, x, y, z) = \Sigma(0, 2, 4, 5, 6, 7, 8, 10, 13, 15)$
- (b)  $F(A, B, C, D) = \Sigma(0, 2, 3, 5, 7, 8, 10, 11, 14, 15)$
- (c)  $F(A, B, C, D) = \Sigma(2, 3, 4, 5, 6, 7, 9, 11, 12, 13)$
- (d)  $F(w, x, y, z) = \Sigma(1, 3, 6, 7, 8, 9, 12, 13, 14, 15)$
- (e)  $F(A, B, C, D) = \Sigma(0, 1, 2, 5, 7, 8, 9, 10, 13, 15)$
- (f)  $F(w, x, y, z) = \Sigma(0, 1, 2, 5, 7, 8, 10, 15)$

5) (i) Convert the following Boolean function from a sum-of-products form to a simplified product-of-sums form.

$$F(w, x, y, z) = \Sigma(0, 1, 2, 5, 8, 10, 13)$$

(ii) Simplify the following expressions to (1) sum-of-products and (2) products-of-sums:

- (a)  $x'z' + y'z' + yz' + xy$
- (b)  $ACD' + C'D + AB' + ABCD$
- (c)  $(A + B + D')(A' + B' + C')(A' + B' + C)(B' + C + D')$
- (d)  $BCD' + ABC' + ACD$

6) Simplify the following Boolean function F, together with the don't-care conditions d, and then express the simplified function in sum-of-products form:

(a)  $F(x, y, z) = \Sigma (0, 1, 4, 5, 6)$ ,  $d(x, y, z) = \Sigma (2, 3, 7)$

(b)  $F(A, B, C, D) = \Sigma (0, 6, 8, 13, 14)$ ,  $d(A, B, C, D) = \Sigma (2, 4, 10)$

(c)  $F(A, B, C, D) = \Sigma (5, 6, 7, 12, 14, 15)$ ,  $d(A, B, C, D) = \Sigma (3, 9, 11)$

(d)  $F(A, B, C, D) = \Sigma (4, 12, 7, 2, 10)$ ,  $d(A, B, C, D) = \Sigma (0, 6, 8)$

7) (i) With the use of maps, find the simplest sum-of-products form of the function  $F = fg$ , where  $f = abc' + c'd + a'cd' + b'cd'$  and  $g = (a + b + c' + d')(b' + c' + d)(a' + c + d')$

(ii) Implement  $F(A, B, C, D) = \Sigma (0, 4, 8, 9, 10, 11, 12, 14)$  using the two-level forms of logic

(a) NAND-AND, (b) AND-NOR, (c) OR-NAND and (d) NOR-OR

8(i) Design a combinational circuit with three inputs and one output.

(a) The output is 1 when the binary value of the inputs is less than 3. The output is 0 otherwise.

(b) The output is 1 when the binary value of the inputs is an even number.

(ii) A majority circuit is a combinational circuit whose output is equal to 1 if the input variables have more 1's than 0's. The output is 0 otherwise. Design a 3-input majority circuit by finding the circuit's truth table, Boolean equation, and a logic diagram.

9(i) Design a combinational circuit that converts a four-bit Gray code to a bit four binary number. Implement the circuit with exclusive-OR gates.

(ii) Design a four-bit combinational circuit 2's complementer. (The output generates the 2's complement of the input binary number.) Show that the circuit can be constructed with exclusive-OR gates. Can you predict what the output functions are for a five-bit 2's complementer?

10) (i) Design a half-subtractor circuit with inputs x and y and outputs  $D_{\text{diff}}$  and  $B_{\text{out}}$ . The circuit subtracts the bits  $x - y$  and places the difference in  $D_{\text{diff}}$  and the borrow in  $B_{\text{out}}$ .

(ii) Design a full-subtractor circuit with three inputs x, y,  $B_{\text{in}}$  and two outputs  $D_{\text{diff}}$  and  $B_{\text{out}}$ . The circuit subtracts  $x - y - B_{\text{in}}$ , where  $B_{\text{in}}$  is the input borrow,  $B_{\text{out}}$  is the output borrow, and  $D_{\text{diff}}$  is the difference.