

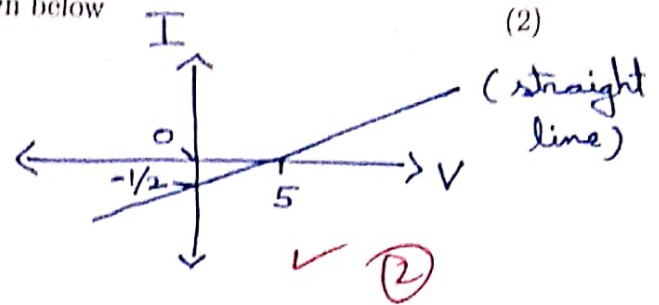
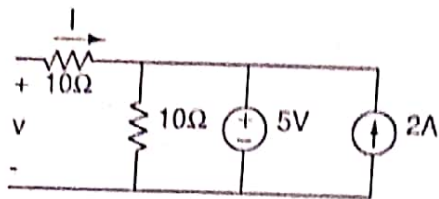


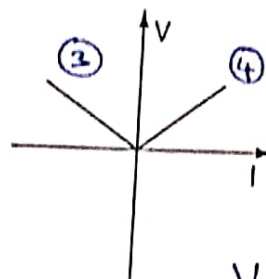1. Plot the I-V characteristic of the circuit shown below



KVL: $V - 10I - 5 = 0 \Rightarrow V = 10I + 5$
 $\Rightarrow I = (V - 5)/10$

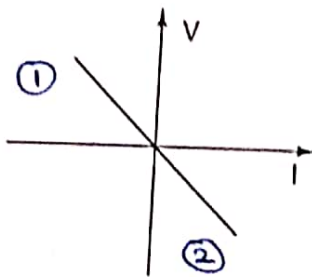
2. The V-I characteristics of two devices are shown below. Mark the regions where the device absorbs/delivers power. Give reasons (2)



①, ②, ③ : delivers power
 ④ : absorbs power

$V \cdot I > 0 \Rightarrow$ absorbs power
 $V \cdot I < 0 \Rightarrow$ delivers power

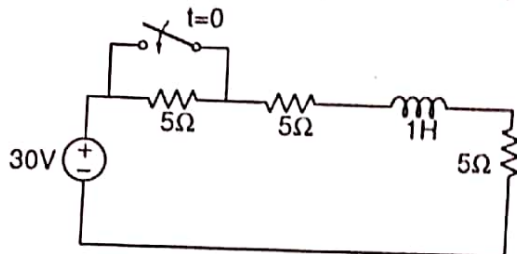
3. Find $v_L(0^+)$, $i_L(0^+)$, $v_L(\infty)$ and $i_L(\infty)$. (4)



ii) $i_L(0^+) = i_L(0^-) = \frac{30}{5+5+5} = 2A$

iv) $i_L(\infty) = \frac{30}{5+5} = 3A$

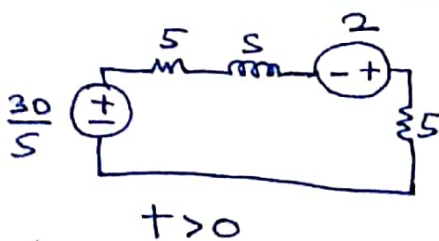iii) $v_L(\infty) = 0V$ ($\because \frac{di_L}{dt} = 0$ @ $t = \infty$)



$I(s) = \frac{\frac{30}{s} + 2}{10 + s}$


$V_L(s) = sI(s) - 2 = \frac{10}{s+10}$

i) $v_L(0^+) = \lim_{s \rightarrow \infty} s V_L(s) = \lim_{s \rightarrow \infty} \frac{10s}{s+10} = 10$




3

4. In the figure below, $I(t) = 2t(u(t) - u(t-1)) + (4-2t)(u(t-1) - u(t-2))$. Plot

(a) $I(t)$, $v_C(t)$ and $v_L(t)$

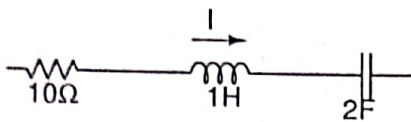

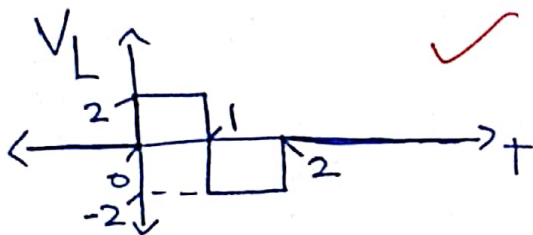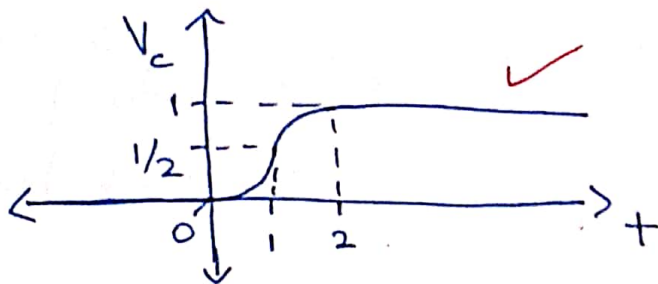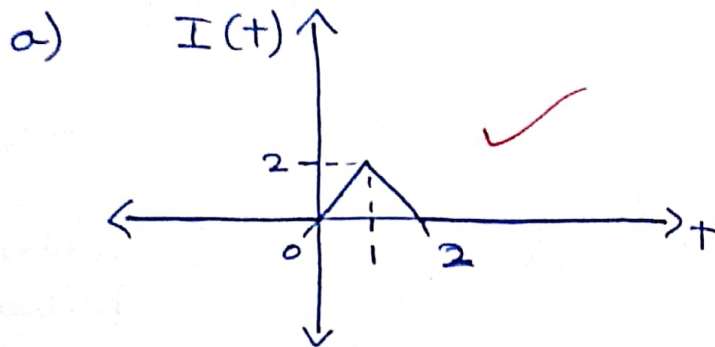(b) The power absorbed/delivered by the inductor as a function of time. (4)



$$v_C(t) = \int_{-\infty}^t \frac{i(\tau)}{2} d\tau$$

$$= \frac{t^2}{2} [u(t) - u(t-1)] + \frac{2-(t-2)^2}{2} [u(t-1) - u(t-2)] + 2u(t-2)$$

$$v_L(t) = L \frac{dI(t)}{dt}$$


$$= 2[u(t) - u(t-1)] - 2[u(t-1) - u(t-2)]$$

b) $P_L = \frac{L}{2} [i(t)^2 - i(0)^2]$

Plot?

$$= 2t^2 [u(t) - u(t-1)] + 2(t-2)^2 [u(t-1) - u(t-2)]$$

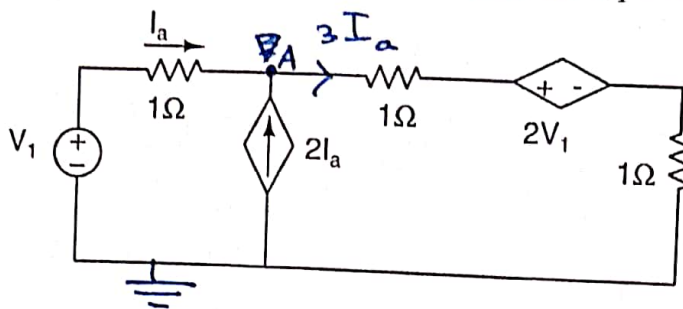5. Write the nodal equations for the following circuit. Put it in a matrix form. Mark the nodes/supernodes clearly and write the equation at each node/supernode. (4)



A: node



$$V_1 - V_A = (1) I_a$$

$$V_A - 3I_a - 2V_1 - 3I_a = 0 \Rightarrow -2V_1 + V_a = 6I_a$$


$$\begin{bmatrix} 1 & -1 \\ -2 & 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_a \end{bmatrix} = \begin{bmatrix} I_a \\ 6I_a \end{bmatrix}$$

$$V_1 = -7I_a$$


Write in terms of V_a, V_b, V_c, V_d .

$$V_A = -8I_a$$

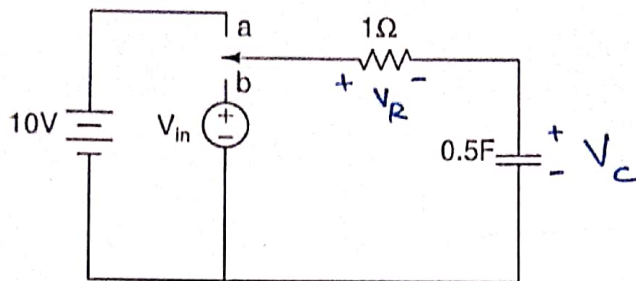6. In the given network, the switch is in position a for a long time. At $t = 0$ it is switched to position b . $V_{in} = e^{-t}u(t)$. (4)



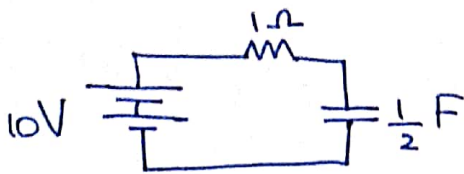
- (a) Draw the circuit with switch at position a and find the capacitor voltage at $t = 0$.



$$\text{At } t=0, i=0 \Rightarrow V_R=0$$

$$\text{Hence, } V_C = 10V$$

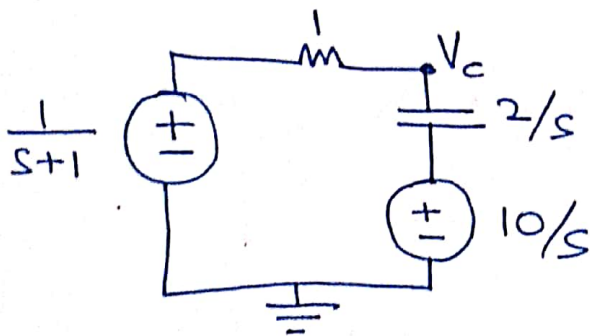- (b) With switch at position b draw the s-domain circuit and determine the voltage across the capacitor as a function of time for $t > 0$.



$$\frac{V_C - 10/s}{2/s} + \frac{V_C - 1/s+1}{1} = 0$$

$$\left(\frac{s+2}{2}\right)V_C = \frac{5s+6}{s+1}$$

$$V_C = \frac{2(5s+6)}{(s+1)(s+2)} = \frac{2}{s+1} + \frac{8}{s+2}$$

$$V_C(t) = 2(e^{-t} + 4e^{-2t})u(t)$$