

# EE2025 (July-Nov 2019) - Tutorial 1 : Transmission Lines

July 2019

Note : All transmission lines can be assumed to be lossless, unless mentioned otherwise.

1. Sinusoidally varying voltage and current can be in general represented as  $Ve^{j\omega t}$  and  $Ie^{(j\omega t+\phi)}$ , where  $V$  and  $I$  are the phasors representing the voltage and current respectively. Find an expression for the average power (over a cycle) in terms of these phasors.
2. The length of a microstrip trace line connecting two components on a chip is 50 cm. A sinusoidal signal of frequency 1 GHz is supplied to the trace at one end. Assuming the velocity of propagation of the signal is  $2 \times 10^8$  m/sec and there are no reflections,
  - (a) Calculate the time taken by the signal to reach the other end of the trace.
  - (b) What is the phase difference between the signal at the two ends of the trace ?
3. Using the concepts of electrostatics, find the capacitance per unit length,  $C$  of
  - (a) parallel wire line, with each wire of radius  $a$  and separated by a distance  $2d$ , where  $a \ll 2d$ .
  - (b) coaxial cable of inner radius  $a$  and outer radius  $b$ .
4. You are required to buy a cable from an electronics shop to connect your dish antenna to your set top box and your set top box to your TV.
  - (a) Write the name of the cable you would buy.
  - (b) Upto what length do you think you can use this cable, in the lumped circuit model and why ?
5. A transmission line with characteristic impedance  $Z_0 = 50 - j5 \Omega$  and propagation constant  $\gamma = 0.2 + j2.5$  /m is connected to a load impedance of  $100 + j50 \Omega$ . Find
  - (a) Reflection coefficient of the line at the load end.
  - (b) Reflection coefficient of the line  $5m$  from the load.
6. A  $300 \Omega$  transmission line is connected to a circuit with an input impedance of  $75 + j35 \Omega$ . Show that the impedance along the line will lie between  $Z_0/\rho$  and  $Z_0\rho$ , where  $\rho$  is the VSWR. Find
  - (a)  $\rho$
  - (b) Maximum impedance seen on the line
  - (c) Minimum impedance seen on the line
7. An RG-59U coaxial cable has a loss of 10 dB per 100 ft of length. A 10 V - 3 A signal is generated using a function generator and connected to one end of the 50 ft long cable. On the other side, the cable is impedance matched to a set top box unit. Find the power delivered to the load.

8. According to the maximum power transfer theorem, maximum time averaged power is transferred from a source with internal impedance  $Z_g$  to a load,  $Z_L$  when  $Z_g = Z_L^*$ . A 50 MHz generator with an internal impedance ( $Z_g$ ) of  $50 \Omega$  is connected to an impedance  $50 - j25 \Omega$ . How would you ensure maximum power transfer in this case using a transmission line of characteristic impedance  $100 \Omega$ , and what should be the minimum length of the transmission line element ?
9. On a  $50 \Omega$  BNC cable line, the reflection co-efficient is measured at the load end to be  $0.7 \angle 30^\circ$ . If the propagation constant of the line is  $20 \angle 89^\circ / m$ , find the impedance seen on the transmission line at a distance of 4 m from the load. (Note : BNC is a very popular type of coaxial cable used for frequencies even up to 4 GHz)
10. Calculate the average power dissipated by each resistor in the circuit shown in Fig. 1.

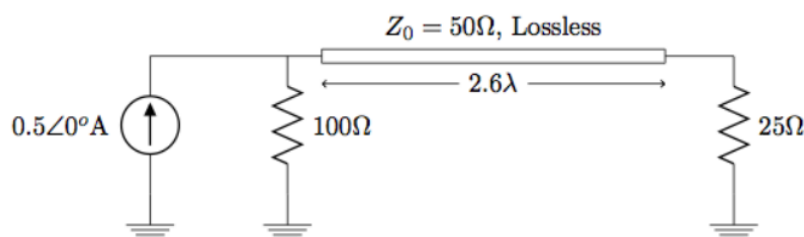


Figure 1: Problem 9

11. Given the system in ( Fig. 2 ) is operating with  $\lambda = 100 \text{ cm}$  and  $Z_0 = 300 \Omega$ . If  $d_1 = 10 \text{ cm}$ ,  $d = 25 \text{ cm}$ , and the system is matched to  $300 \Omega$ , find  $Z_L$ ?

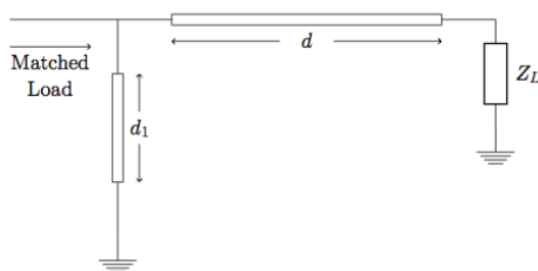


Figure 2:

12. The two-wire lines shown in Fig. 3 are all lossless and have  $Z_0 = 200 \Omega$ . Find the possible values of  $d$  and  $d_1$  to provide a matched load if  $\lambda = 100 \text{ cm}$ . (Note that the un-shaded and shaded conductor are both parts of the same transmission line, for example they can be the inner and outer conductor of a coaxial cable.)
13. Approximate distributed circuit models of (lossless) a lossless transmission operating in high frequency modes is shown in Fig. 4. Note that  $L$  has units  $H \cdot m$ ,  $C$  has units  $F \cdot m$ ,  $L_0$  has units  $H/m$  and  $C_0$  has units  $F/m$ . Obtain expressions for the propagation constant  $\beta$  and the characteristic impedance  $Z_0$  of the line for both circuits at frequency  $\omega$ .

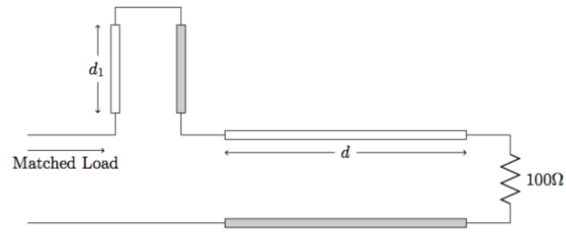


Figure 3:

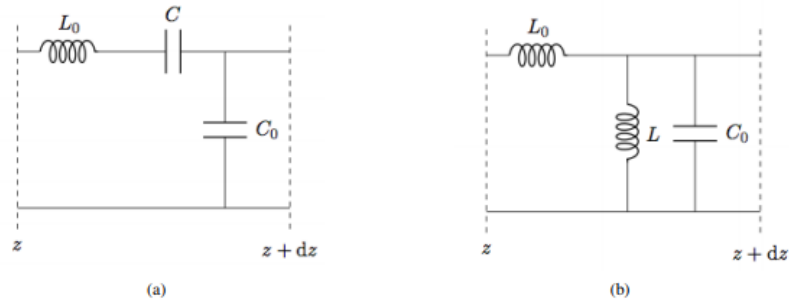


Figure 4:

14. For the transmission line represented in Fig. 5, calculate the potential developed across the  $80\Omega$  resistor for (a)  $f = 60Hz$ , (b)  $f = 1MHz$ , (c) Repeat part (a) with length  $10^7m$  instead of  $80m$ .

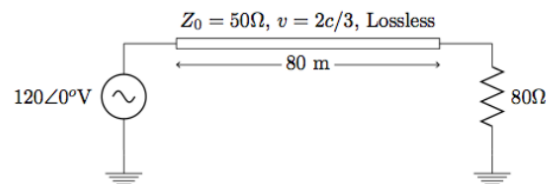


Figure 5: