 


EE2001-Tutorial 9
Date: 10th April 2018
Memory and Programmable Logic

- 1) (a) Using 64×8 ROM chips with an enable input, construct a 512×8 ROM with eight chips and a decoder.
- (b) A ROM chip of $4,096 \times 8$ bits has two chip select inputs and operates from a 5-V power supply. How many pins are needed for the integrated circuit package? Draw a block diagram, and label all input and output terminals in the ROM.
- 2) The 32×6 ROM, together with the 2^0 line, as shown, converts a six-bit binary number to its corresponding two-digit BCD number. For example, binary 100001 converts to BCD number 011 0011 (decimal 33). Specify the truth table for the ROM.




- 3) Specify the size of a ROM (number of words and number of bits per word) that will accommodate the truth table for the following combinational circuit components:
- (a) a binary multiplier that multiplies two 4-bit binary words,
- (b) a 4-bit adder-subtractor,
- (c) a quadruple two-to-one-line multiplexer with common select and enable inputs, and
- (d) a BCD-to-seven-segment decoder with an enable input.
- 4) Tabulate the PLA programming table for the four Boolean functions listed below. Minimize the numbers of product terms.
- (a) $A(x, y, z) = \Sigma(1, 3, 5, 6)$
- (b) $B(x, y, z) = \Sigma(0, 1, 6, 7)$
- (c) $C(x, y, z) = \Sigma(3, 5)$
- (d) $D(x, y, z) = \Sigma(1, 2, 4, 5, 7)$
- 5) Tabulate the truth table for an 8×4 ROM that implements the following Boolean functions:
- (a) $A(x, y, z) = \Sigma(0, 3, 4, 6)$
- (b) $B(x, y, z) = \Sigma(0, 1, 4, 7)$
- (c) $C(x, y, z) = \Sigma(1, 5)$
- (d) $D(x, y, z) = \Sigma(0, 1, 3, 5, 7)$
- Considering now the ROM as a memory. Specify the memory contents at addresses 1 and 4.

6) (a) Derive the PLA programming table for the combinational circuit that squares a three-bit number. Minimize the number of product terms.

(b) Derive the ROM programming table for the combinational circuit that squares a 4-bit number. Minimize the number of product terms.

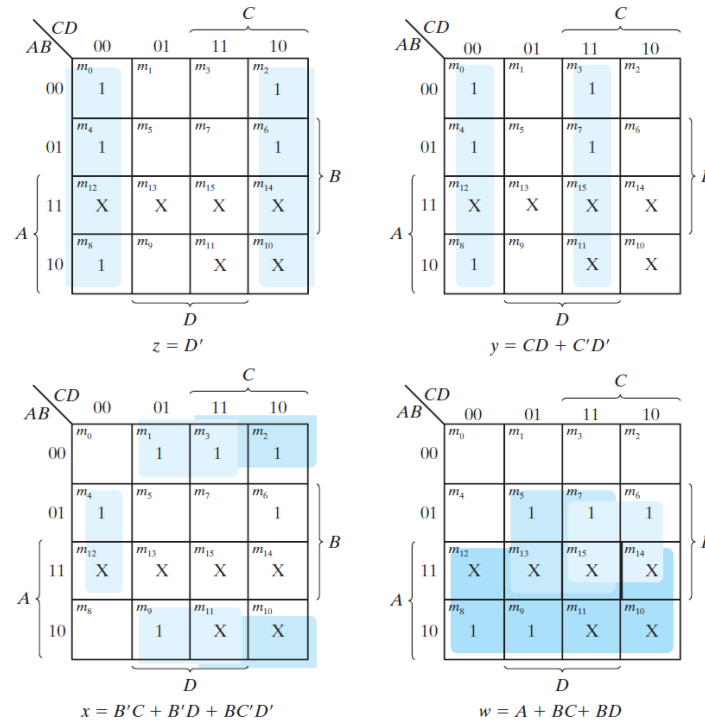7) List the (a) PLA and (b) PAL programming tables for the BCD to excess-3 code converter whose Boolean functions are simplified as shown.




8) Draw a PLA circuit to implement the functions

(a) $F1 = A'B + AC + A'BC'$

(b) $F2 = (AC + AB + BC)'$

9) Using the given registered macrocell, show the fuse map for a sequential circuit with two inputs x and y and one flip-flop A described by the input equation

$D_A = x \text{ XOR } y \text{ XOR } A$

 

10) Modify the given PAL diagram by including three clocked D-type flip-flops between the OR gates and the outputs (as in a registered macrocell). The diagram should conform with the block diagram of a sequential circuit. The modification will require three additional buffer-inverter gates and six vertical lines for the flip-flop outputs to be connected to the AND array through programmable connections.

Using the modified registered PAL diagram, show the fuse map that will implement a three-bit binary counter with an output carry.

