 


Tutorial 5

- Design a 3-bit counter which counts in the sequence:
001, 011, 010, 110, 111, 101, 100, 001,...
a) Use clocked D flip-flops.
b) Use clocked T flip-flops.
- Repeat above Problem for the sequence using clocked JK flip-flops.
001, 100, 101, 111, 110, 010, 011, 001,...
- Using clocked T flip-flops design a decade counter which counts in the 6-3-1-1 code sequence
- (a) For the following sequential network, find the next-state equation or map for each flip-flop.
Using these next-state equations or maps, construct a (Moore) state table and graph for the network.
(b) What is the output sequence when the input sequence is $X \sim 01100$?
(c) Draw a timing diagram for the input sequence in (b). Show P_c , X , A , B , and Z . Assume that the input changes between clock pulses.



- Design a four-bit shift register with parallel load using D flip-flops. There are two control inputs: shift and load. When shift = 1, the content of the register is shifted by one position. New data are transferred into the register when load = 1 and shift = 0. If both control inputs are equal to 0, the content of the register does not change.
- A flip-flops has a 3 ns delay from the time the clock edge occurs to the time the output is complemented. What is the maximum delay in a 10-bit binary ripple counter that uses these flip-flops? What is the maximum frequency at which the counter can operate reliably?
- Design a serial 2's complementer with a shift register and a flip-flop. The binary number is shifted out from one side and it's 2's complement shifted into the other side of the shift register